

Vansh Patpatia


47, N

[Signature]

Q 5.)


- i) i) Switch on Digital Multimeter.
- ii) Set the measurement knob to the correct measurement type in this case voltage.
- iii) Insert the poles into correct connection.
- iv) Measure the current using multimeter.

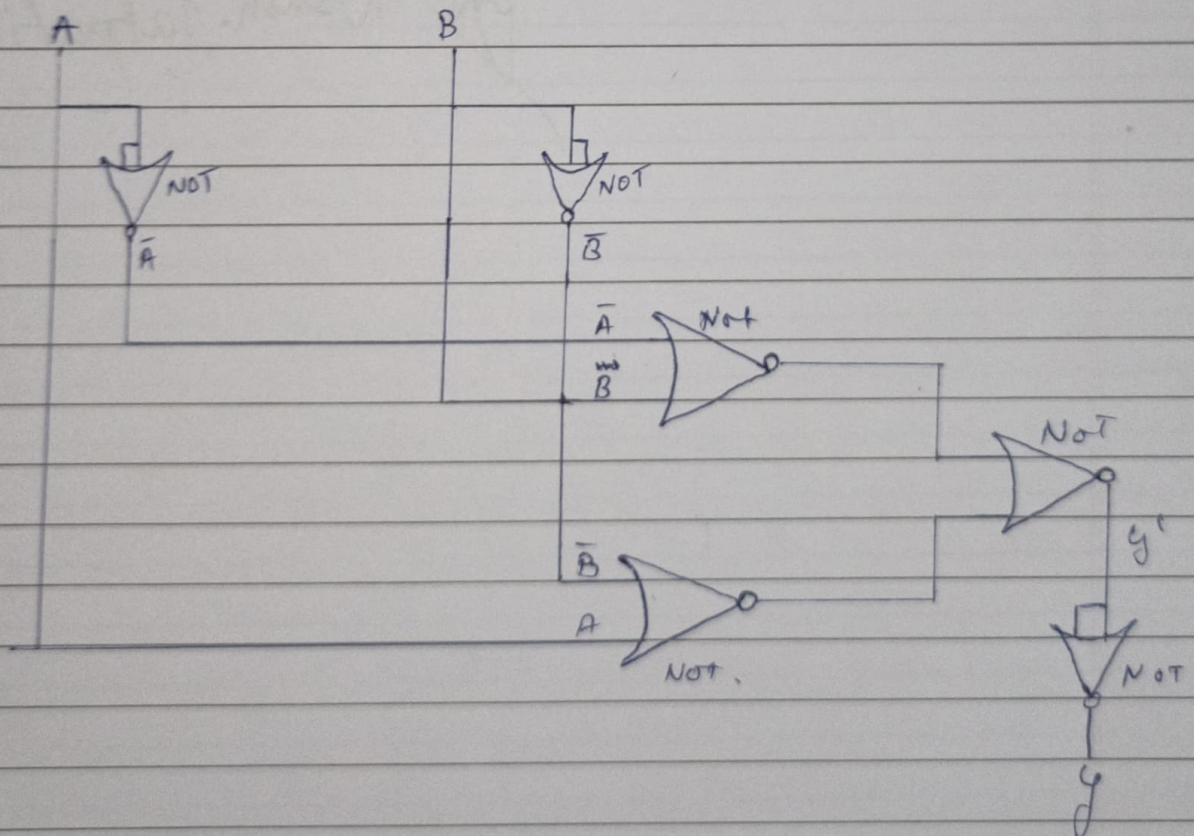Q 2.) $y = A\bar{B} + \bar{A}B$ (EX-OR Using NOR Gate)



Truth Table.

A	B	\bar{A}	\bar{B}	$A\bar{B}$	$\bar{A}B$	y
0	0	1	1	0	0	0
1	0	0	1	1	0	1
0	1	1	0	0	1	1
1	1	0	0	0	0	0

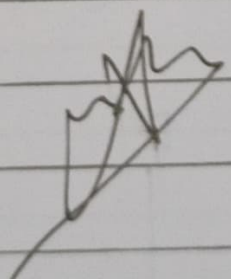

Vansh Patpatia